
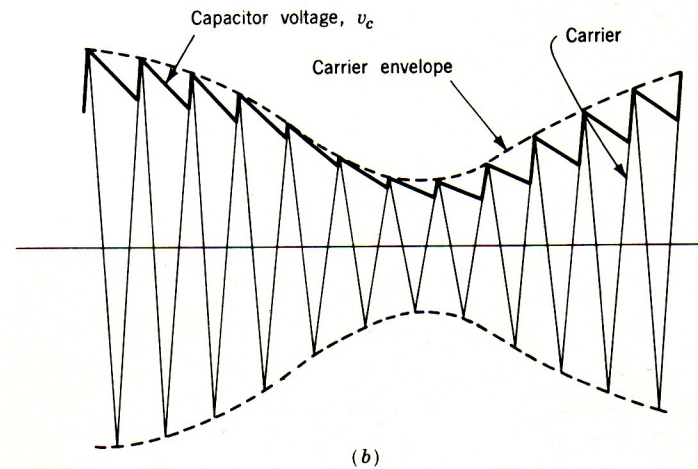


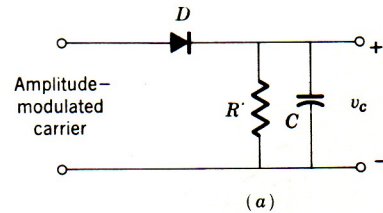


Fermilab

Mixers
Frequency Conversion
and
Applications



Ralph J. Pasquinelli



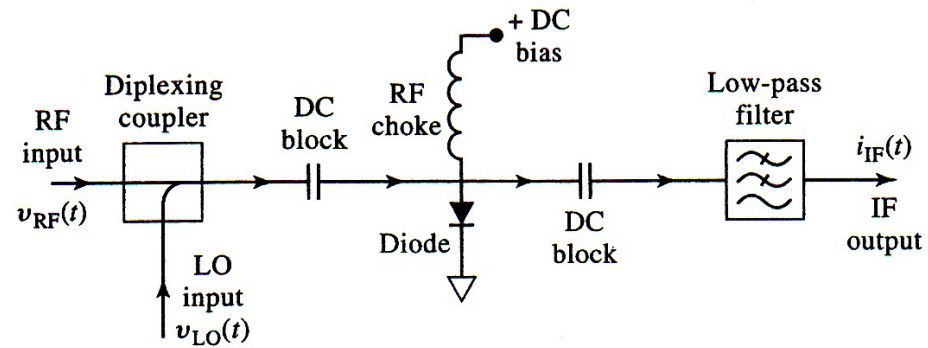a) Diode demodulator for AM b) input and output waveforms



(a)

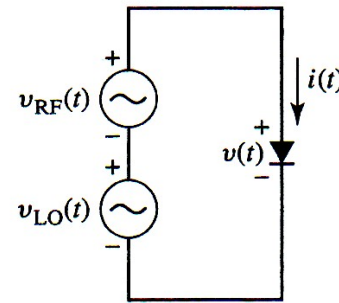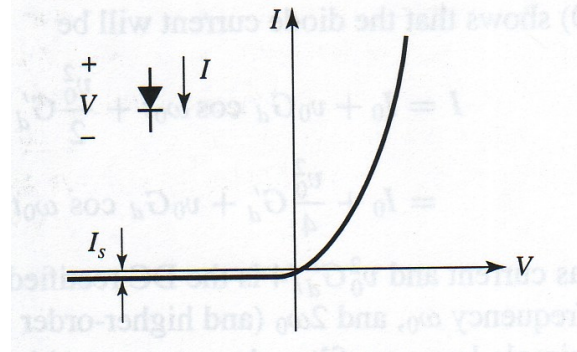

(b)

a) Basic Diode Mixer b) equivalent circuit



Fermilab

Frequency Conversion

Let the LO and IF be represented by

$$v_{LO}(t) = \cos 2\pi f_{LO} t$$

$$v_{IF}(t) = \cos 2\pi f_{IF} t$$



the mixer multiplies the two

$$v_{RF}(t) = K v_{LO}(t) v_{IF}(t) = K \cos 2\pi f_{LO} t \cos 2\pi f_{IF} t$$



$$v_{RF} = \frac{K}{2} [\cos 2\pi (f_{LO} - f_{IF}) t + \cos 2\pi (f_{LO} + f_{IF}) t] \text{ UP-Conversion}$$

Likewise
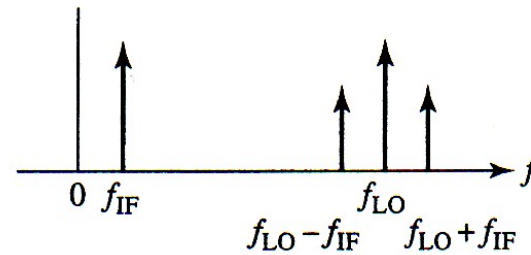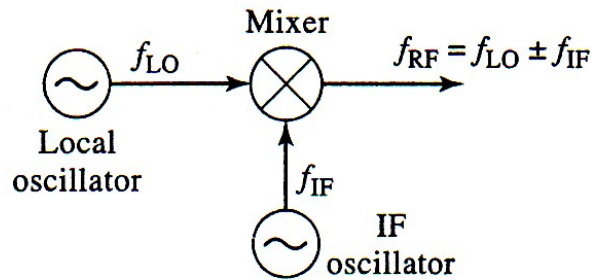
$$v_{IF} = \frac{K}{2} [\cos 2\pi (f_{RF} - f_{LO}) t + \cos 2\pi (f_{RF} + f_{LO}) t] \text{ Down-Conversion}$$



(a)

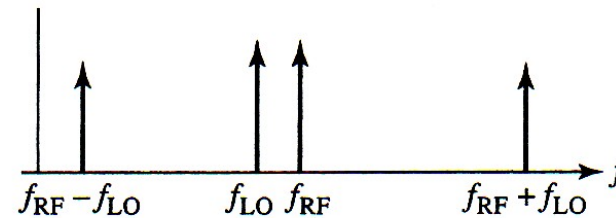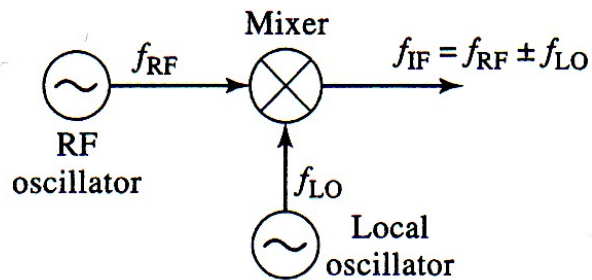

(b)


Frequency Conversion. a) Up-conversion b) Down Conversion




RJP 1/03/02

Multiplying or "Mixing" signals
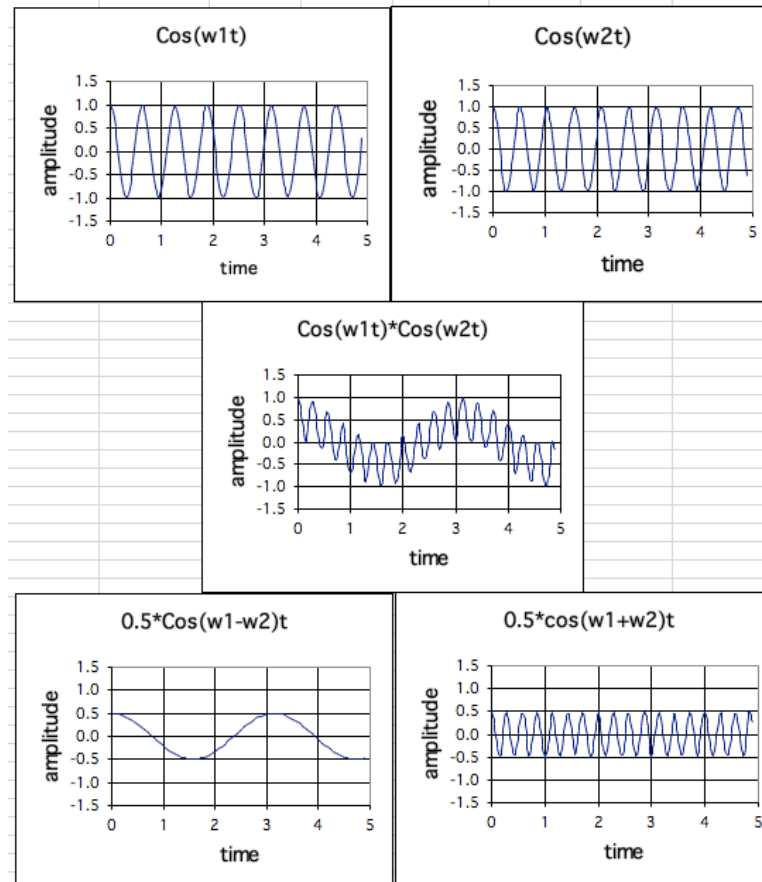
$$\text{Cos}(w_1t) * \text{Cos}(w_2t) = 0.5 * [\text{Cos}(w_1 - w_2)t + \text{Cos}(w_1 + w_2)t]$$




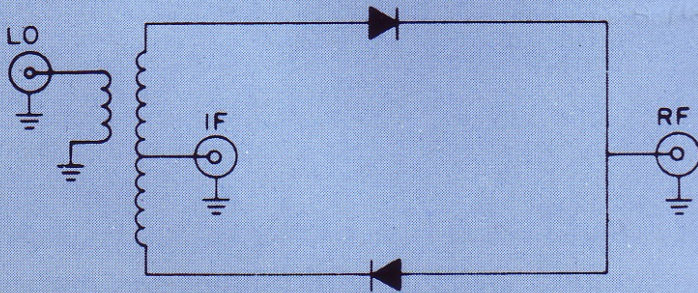

Schematic of
Single Balanced Mixer

Advantages: Simple circuit

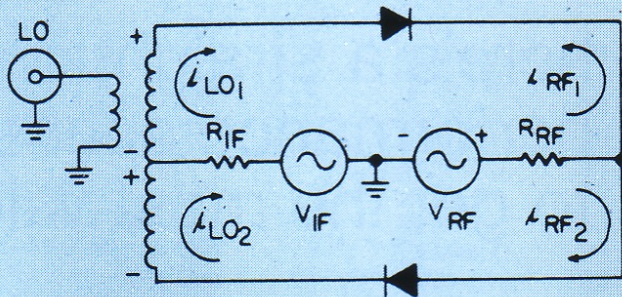Disadvantage: no isolation between IF and RF ports




Currents in
Single Balanced Mixer



Fermilab

Double Balanced Mixer (DBM)

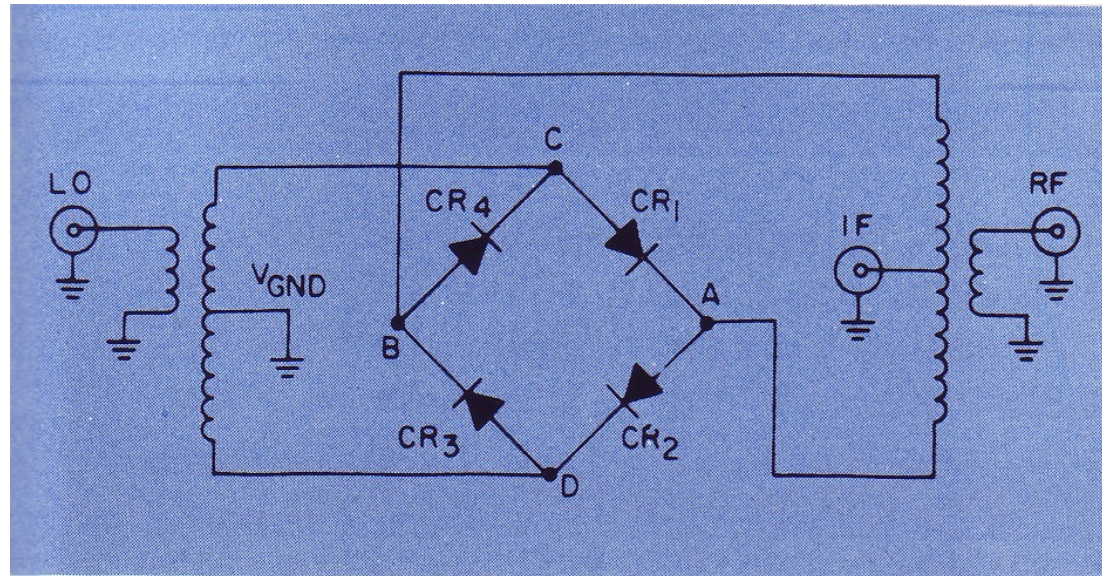


Advantage: good isolation between all ports




Conversion Loss is the measure of efficiency of frequency translation, i.e. the factor K mentioned previously expressed in dB

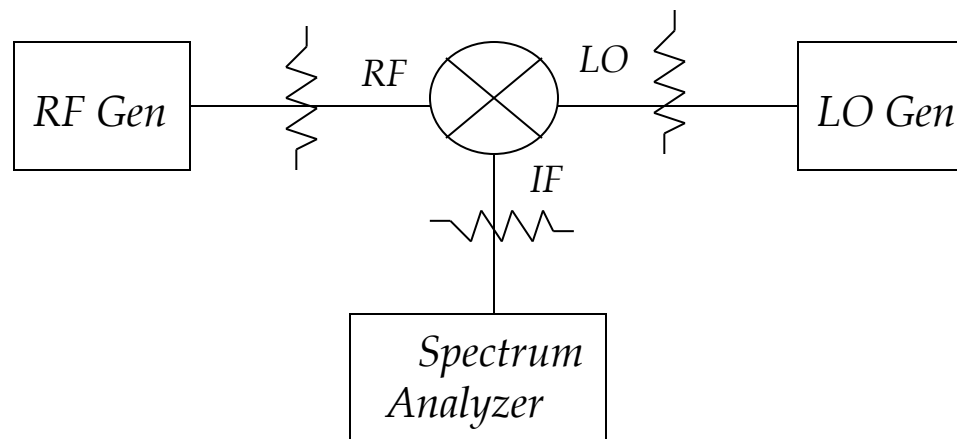*Mixers operate at various power levels ranging mostly between +7 and +23 dBm on the LO port
Pads on Ports insure good match*





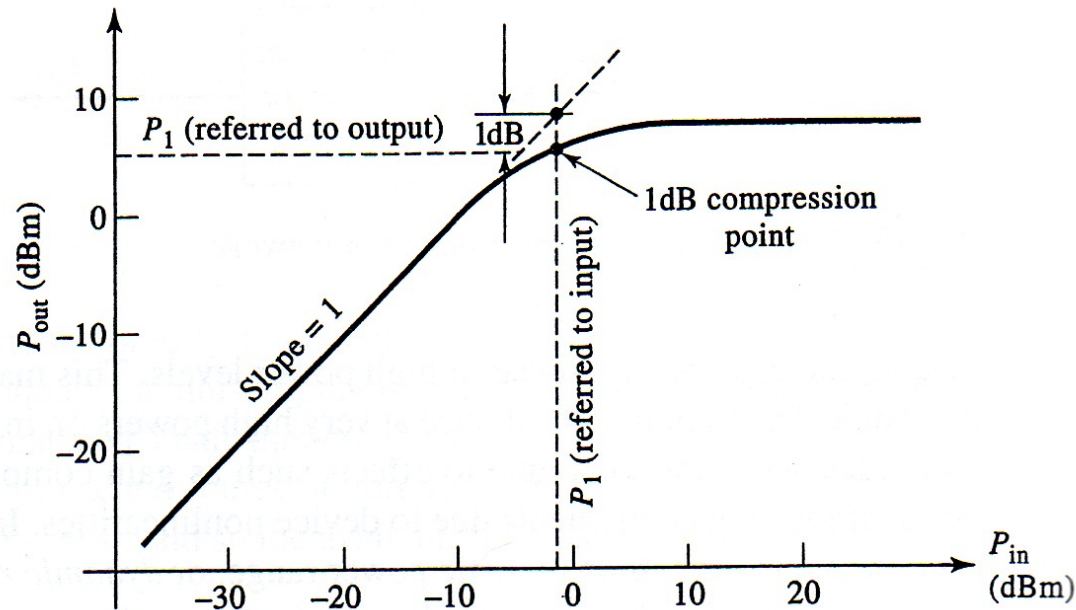Linearity is the specification of how closely the input to output translation follows a slope of 1
1 dB compression is point where conversion loss becomes 1 dB greater than a linear response






Fermilab

3rd Order Intercept

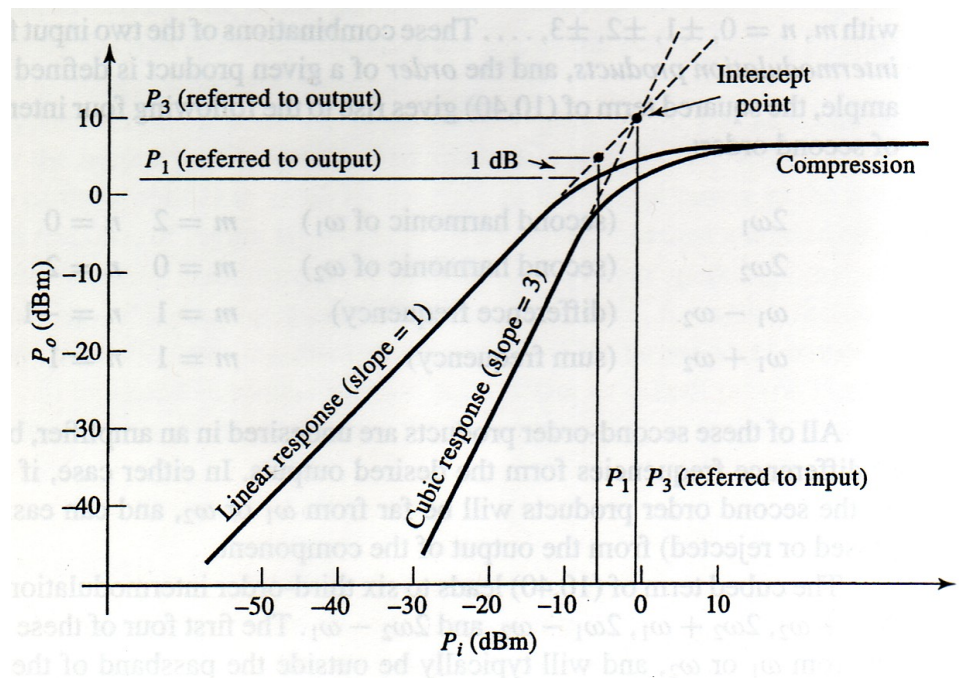When 2 signals at the mixer input generate third order products
($2f_1-f_2$) or ($2f_2-f_1$)




R. J. Pasquinelli



Fermilab

3rd Order Intercept

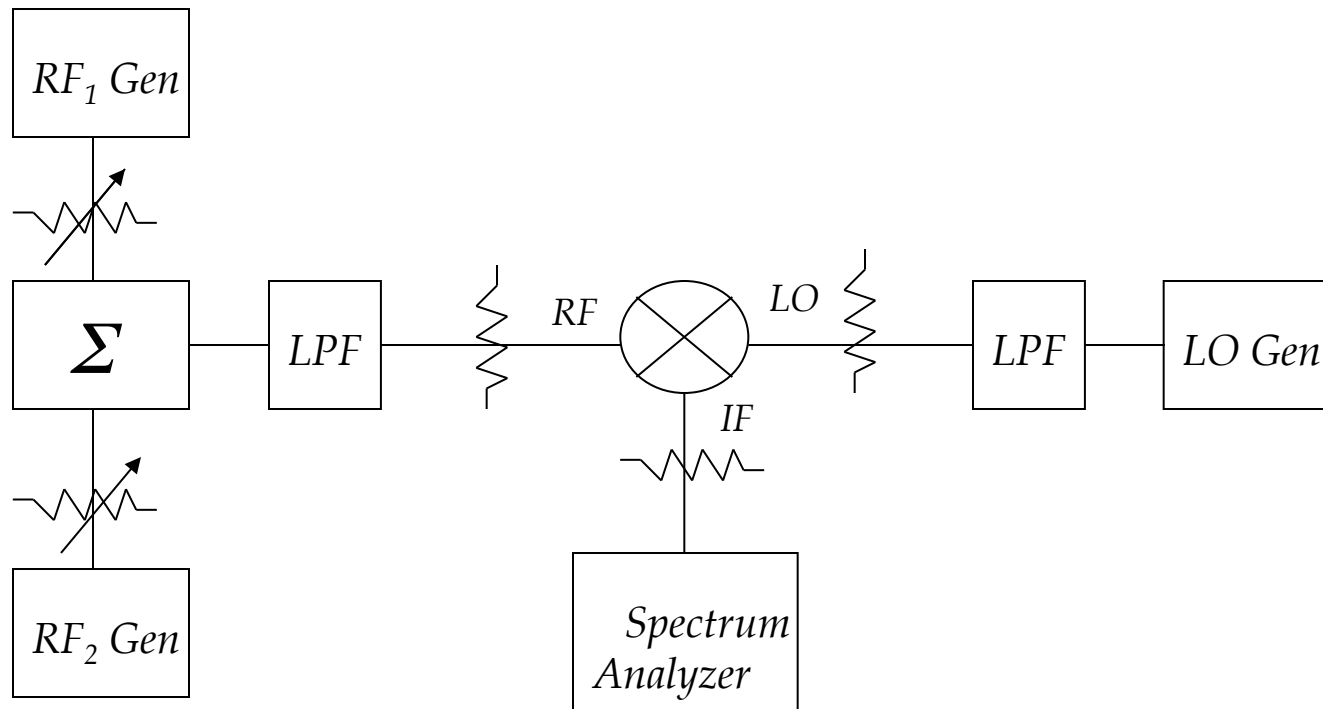
*Measurement setup for third order products
($2f_1-f_2$) or ($2f_2-f_1$)*





Fermilab

Isolation measurement of DBM

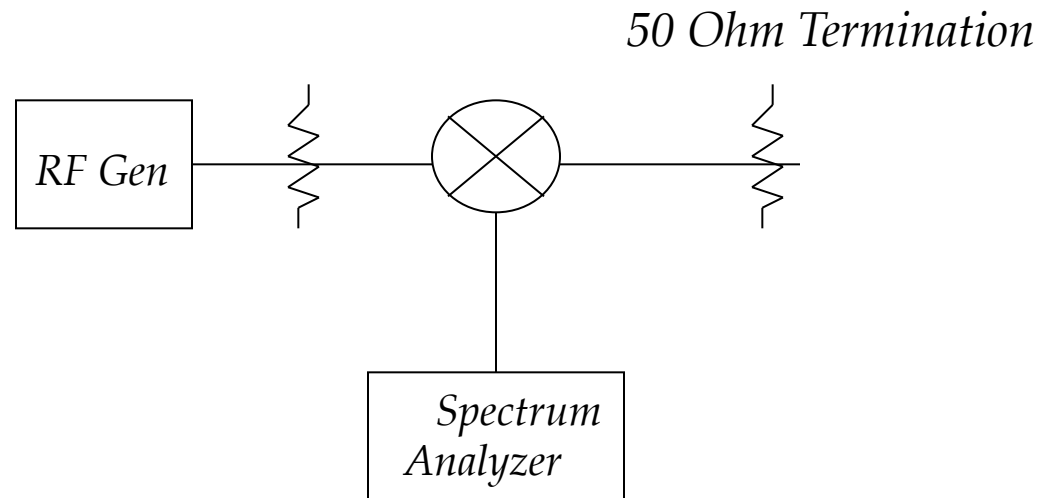


pad on generator insures good match



Fermilab

DBM as phase detector

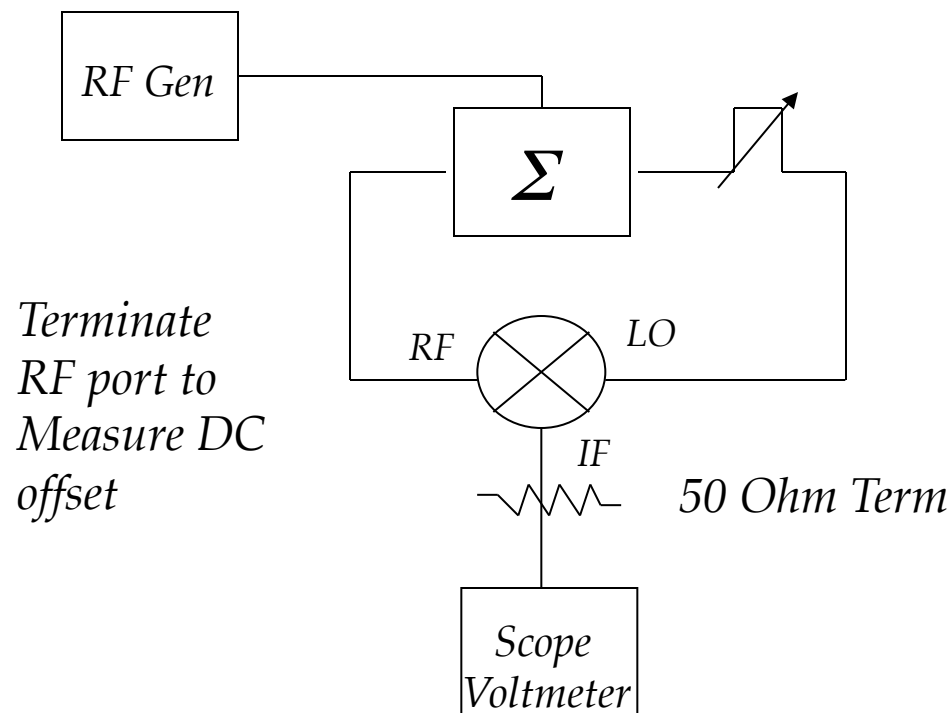Measurement setup for phase detector and DC offset



R. J. Pasquinelli



Fermilab

DBM as current controlled attenuator

Measurement setup for current controlled attenuator

